

1 Study of three-phase autonomous voltage inverter

1.1 Objective

Study of electromagnetic processes, common characteristics and energy characteristics of a three-phase autonomous voltage inverter (AVI).

1.2 Description of the laboratory setup

The laboratory setup includes the following modules: “Frequency converter” /Преобразователь частоты/, “Load” /Нагрузка/, “Power module” /Модуль питания/, “Thyristor converter” /Тиристорный преобразователь/, “Measuring module” /Модуль измерительный/, “Multimeters” /Мультиметры/, “Power meter” /Измеритель мощности/, a two-channel oscilloscope.

The Frequency Converter module provides conversion of alternating voltage 220 V with a frequency of 50 Hz into three-phase voltage with adjustable voltage and frequency values.

The front panels of the “Frequency Converter” and “Load” modules are shown in Fig. 1,2 respectively. The Frequency Converter module (see Fig. 1) contains:

- frequency converter E2-MINI-SP5L;
- power connectors for supplying single-phase input voltage A and N and removing output voltage $A1$, $B1$ and $C1$;
- power connectors for rectified voltage U_d : “+” connector $X5$ and “—” connector $X6$;
- potentiometer for setting the control signal $PR1$ for simultaneous regulation of the frequency and output voltage;
- button $SB1$ “Reset”/Сброс/ to reset the error after the protection has been triggered;
- switch $SA1$, changing the phase sequence (direction of rotation);
- frequency meter for measuring the frequency at the output of the AVI;
- LEDs signaling power supply, normal operation and protection activation;
- voltage (ДН) and current (ДТ) sensor for oscillography and measurements of voltages and currents in the circuit.

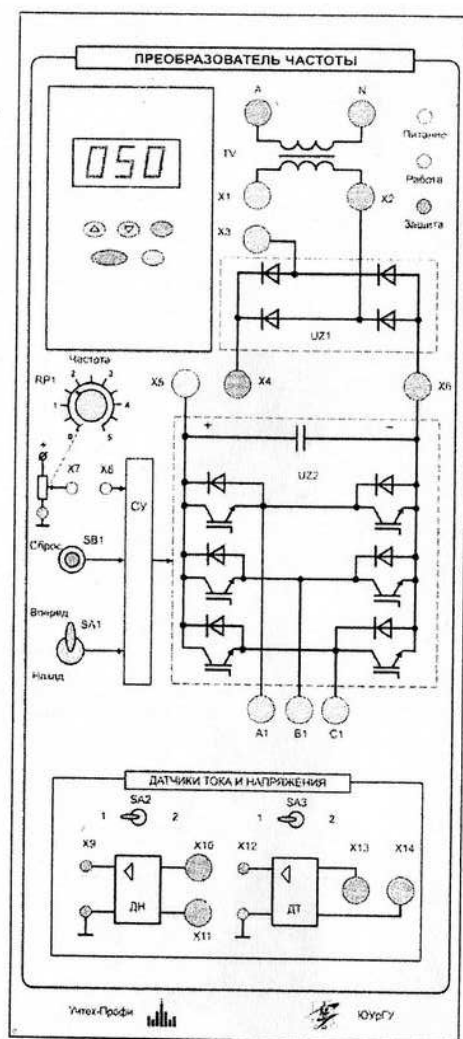


Рис. 1: Frequency converter

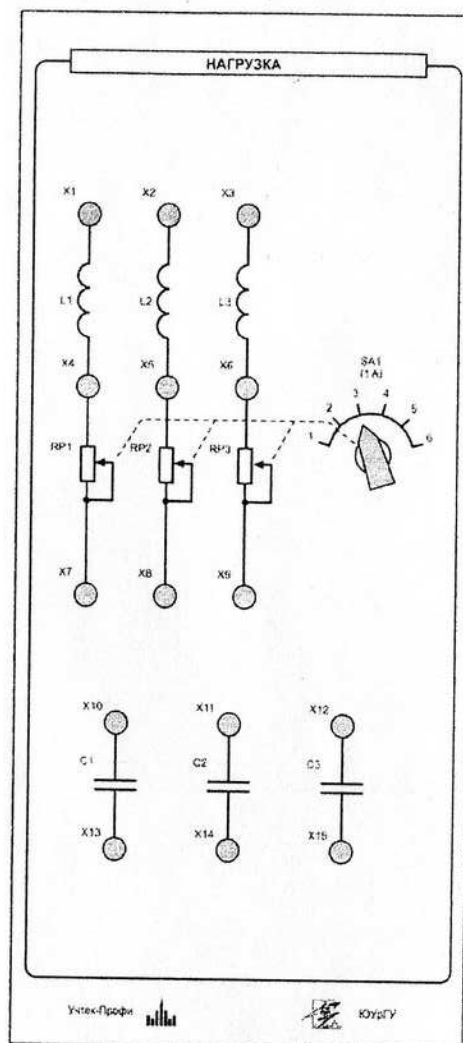


Рис. 2: Load

The module is powered from the AC mains through an isolation transformer *TV*, which provides potential isolation from the mains.

The Frequency Converter module consists of two units (see Fig. 1). The first unit of the frequency converter (FC) is an uncontrolled diode rectifier (*UZ1*), made using a single-phase bridge circuit. The second unit is a three-phase AVI made on IGBT transistors (*UZ2*). A capacitive filter is enabled at the *UZ2* input.

In this work, we study the second unit - a three-phase autonomous voltage inverter.

The Frequency Converter module contains current (ДТ) and voltage (ДН) sensors, which are used for oscillography and measurement of voltages and currents in the circuit. Voltage signals are supplied to connectors *X10* and *X11*, and current signals are supplied to connectors *X13* and *X14*. Connectors *X9*, *X12* and the common wire "⊥" are used to connect the

output circuits ΔT and ΔH to the oscilloscope or the input/output module. Voltage sensor conversion coefficient $k_v = 40V/V$, current sensor conversion coefficient $k_c = 0.25A/V$. The actual voltage and current values are determined by multiplying the values measured using an oscilloscope by the corresponding sensor factor.

Using toggle switches $SA2$ and $SA3$ of the “Frequency Converter” module, the bandwidth of the sensors is changed, which allows you to observe either the PWM signal (position “2”) or its first harmonic (position “1”) on the screen of an oscilloscope or computer.

The “Frequency Converter” module is powered through sockets A and N of the three-phase alternating voltage source through the $QF2$ circuit breaker located in the power module.

The “Load” module (see Fig. 2), containing reactors ($L1 - L3$), resistors ($RP1 - RP2$) and capacitors ($C1 - S2$) is used as an AVI load.

In the “Load” module, only the active phase resistances ($RP1 - RP$) are regulated, and the reactive elements remain unchanged. Regulation is made by switch $SA1$. The resistor values corresponding to the switch positions are given in table 1.

Switch position $SA1$	1*	2	3	4	5	6
Load Resistance (Ohm)	100	200	400	600	1000	1600

Таблица 1

Note: “*” marks prohibited switch positions. The inductances ($L1 - L3$) are $80mH$, and the capacitances ($C1 - C2$) are $10\mu F$.

To obtain a three-phase active-inductive load, it is necessary to install jumpers between sockets $X7 - X8$ and $X8 - X9$ (zero load point).

1.3 The procedure for turning the lab stand on and off

1. Assemble an experimental scheme for performing laboratory work.
2. In the “Frequency Converter” module, set toggle switch $SA1$ (“Rotation direction”) to the middle position, frequency setting potentiometer $RP1$ to the zero position.
3. Set switch $SA1$ on the “Load” module to the position of maximum resistance (far right position).
4. Turn on the machine $QF1$ of the “power module of the stand”, turn on the machine $QF2$ of the “power module”.

5. Turn on the “Power” toggle switch of the “Power Meter” module.
6. In the “Frequency Converter” module, switch toggle switch SA1 to the upper position. The “Operation” LED will light up.
7. Use potentiometer $RP1$ to set the required frequency f and the corresponding load voltage. In this case, the law $U_{lin}/f = const$ is satisfied.
8. Set switch $SA1$ to the required resistance on the “Load” module.

Shutdown procedure: turn off the $SA1$ toggle switch of the “Frequency Converter” module, and then the “Power” toggle switch of the “Power Meter” module, turn off the $QF2$ “Power Module” circuit breaker.

1.4 Assignment and guidelines

1. Preliminary homework:

- (a) study the topic of the course: “Autonomous voltage inverters”, “Energy indicators of rectifiers”, the content of this work and be ready to answer all test questions;
- (b) calculate the modulation coefficient μ for a given option. It is recommended to determine the modulation depth from the relation

$$\mu = \frac{U_{lin\ m}}{U_d} = \frac{f}{f_{max}} \quad (1)$$

where $U_{lin\ m}$ is the amplitude value of the line-line voltage at the output of the AVI;

U_d – constant voltage at the input of the AVI;

f, f_{max} are the specified and maximum frequency at the output of the AVI, respectively;

- (c) calculate for a given option the highest effective values of the first harmonic of line $U_{L\ lin(1)max}$ and phase $U_{L\ ph(1)max}$ voltages on the load for different modulation methods:
 - when generating average voltages at the terminals relative to the midpoint of the power source

$$U_{L\ lin(1)max} = \frac{\sqrt{3} \cdot U_d}{2\sqrt{2}}, \quad U_{L\ ph(1)max} = \frac{U_d}{2\sqrt{2}} \quad (2)$$

- when generating phase voltages using a space vector

$$U_{L\,lin(1)max} = \frac{U_d}{\sqrt{2}}, \quad U_{L\,ph(1)max} = \frac{U_d}{\sqrt{6}} \quad (3)$$

- (d) calculate the RMS-values of the first harmonic of line-line $U_{L\,lin(1)}$ and phase $U_{L\,ph(1)}$ voltages on the load for different modulation methods at a given frequency f and the calculated modulation coefficient μ :

$$U_{L\,lin(1)} = \mu U_{L\,lin(1)max}, \quad U_{L\,ph(1)} = \mu U_{L\,ph(1)max} \quad (4)$$

2. Experimental study of three-phase AVI:

- (a) assemble a circuit for studying a three-phase AIN when operating on an active-inductive load in accordance with Fig. 3. Additional jumpers and measuring instruments connected to the circuit are shown with a dashed line.

In table 2 shows measuring instruments, and table 3 current and voltage sensors used in laboratory work, in accordance with the accepted designations on the circuit diagram (see Fig. 3).

Measured quantities	Device designation	Measurement limit	Device location (module name)
Direct voltage at the input of the AVI U_d	<i>PV1</i>	$= 1000V$	Multimeters
Direct current at the AVI input I_d	<i>PA1</i>	—	Measuring module
RMS-value of the first harmonic of the phase voltage $U_{L\,ph(1)}$ and phase current $I_{L\,ph(1)}$ at the output of the AVI	<i>PW1</i>	$U_{L\,ph(1)} \approx 300V;$ $I_{L\,ph(1)} \approx 2A$	Power meter

Таблица 2

Set the toggle switches *SA2* and *SA3* of the voltage (ДН1 – ДН2) and current (ДТ1 – ДТ2) sensors in the “Thyristor Converter” and “Frequency Converter” modules to position “2” (the filter is off). Set the required measurement limits on measuring instruments according to table 2;

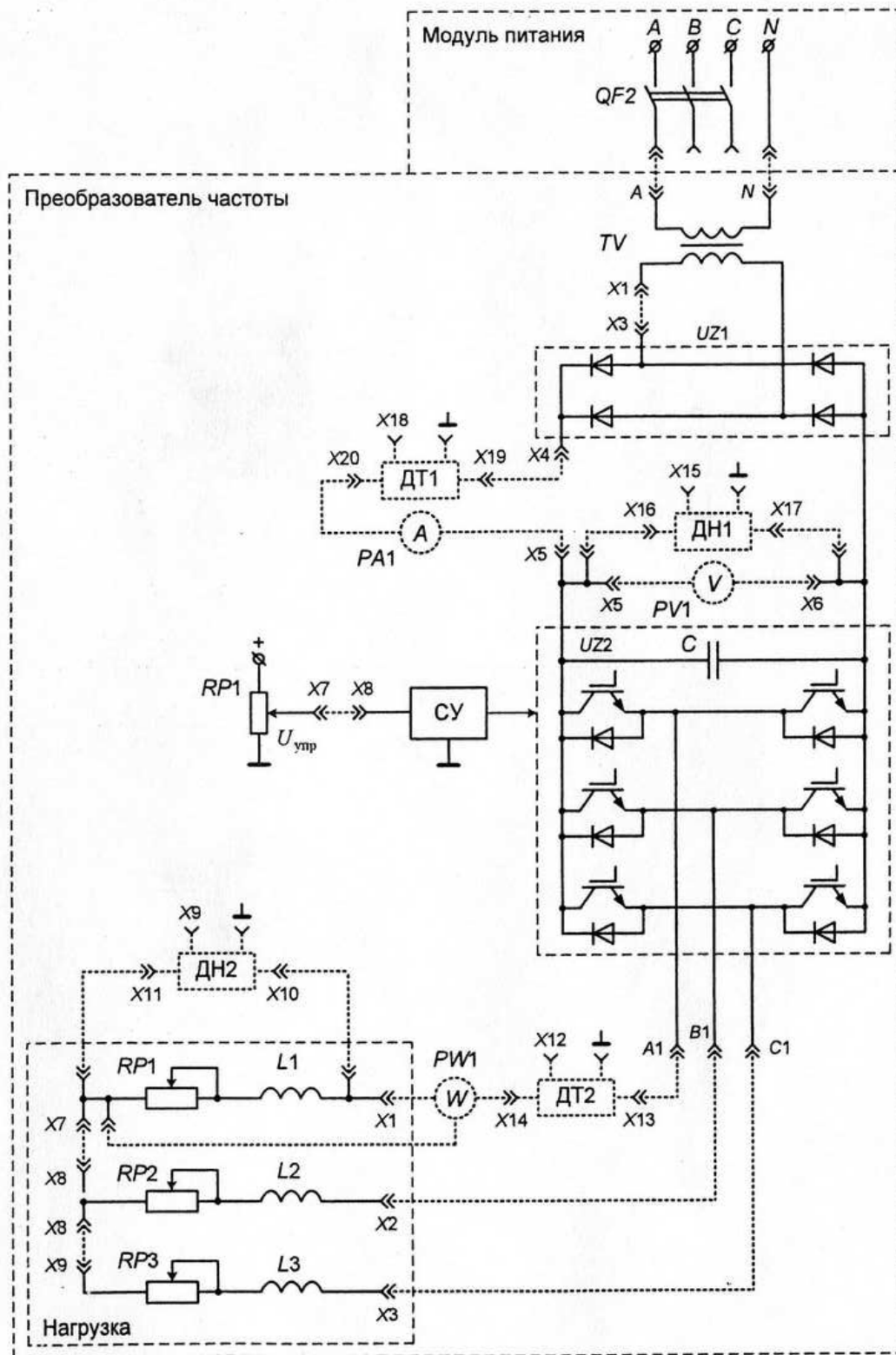


Рис. 3: Schematic diagram for studying an autonomous voltage inverter when operating on an active-inductive load

- (b) take oscillograms of the first harmonic of the phase voltage $u_{Lph(1)}$ and current $i_{Lph(1)}$ at the output of the AVI using an oscilloscope

for a given load resistance R_L and control frequency f . To do this, connect the oscilloscope to the ДТ2 current sensor (channel $CH2$ – socket $X12$, connect the oscilloscope corpus to socket “⊥” ДТ2) and voltage sensor ДН2 (channel $CH1$ – socket $X9$). Perform the necessary operations specified in the order in which the lab stand was turned on. Use potentiometer $RP1$ in the “Frequency Converter” module to set the specified value of control frequency f , and switch $SA1$ in the “Load” module set the specified value of load resistance R_L .

Measured signal	Device designation	Device (module name)	location
Instantaneous voltage value at the AVI input u_d	ДН1	Thyristor converter	
Instantaneous current value at the AVI input i_d	ДТ1	Thyristor converter	
Instantaneous value of phase voltage at the output of the AVI u_{Lph}	ДН2	Frequency converter	
Instantaneous value of the phase current at the output of the AVI i_{Lph}	ДТ2	Frequency converter	

Таблица 3

First, look at the oscillograms with a wide bandwidth of the sensors (position “2” of the toggle switches $SA2$ and $SA3$ of the “Frequency Converter” module), and then, switching the toggle switches $SA2$ and $SA3$ of the sensors to position “1”, sketch the oscillograms of the first harmonics of the phase voltage $u_{Lph(1)}$ and current $i_{Lph(1)}$. Pay attention to the phase shift between them (angle φ), as well as to the change in phase shift when the control frequency f changes. Don’t forget to define the voltage, current and time scales taking into account the sensor coefficients;

- (c) take oscillograms of voltage u_d and current i_d at the input of the AVI at the same values of load resistance R_L and control frequency f . To do this, connect the oscilloscope to the current sensor ДТ1 (channel $CH2$ - socket $X18$, connect the oscilloscope body to socket “⊥” ДТ1) and the voltage sensor ДН1 (channel $CH1$ – socket $X15$).

Explain the pulsed nature of the current consumed by the AVI at the input;

- (d) take the regulating characteristics $U_{Lph(1)} = F(f)$, $\mu = F(f)$ and energy characteristics $P_d = F(f)$, $P_L = F(f)$, $S_L = F(f)$, $\cos \varphi_L = F(f)$, $\eta_L = F(f)$ of an autonomous voltage inverter when regulated according to the law $U/f = \text{const}$ and a given value R_L . Change the frequency in the range of 10 – 50 Hz. To increase the measurement accuracy by eliminating interference, connect the zero point of the “Load” module (socket $X7$) to ground (socket N of the “Power module”).

Record the following values and enter them into the table 4:

- f – frequency at the output of the AVI;
- U_d, I_d - constant voltage and current at the input of the AVI, respectively;
- $U_{Lph(1)}, I_{Lph(1)}$ are the RMS-values of the first harmonic of the phase voltage and current at the output of the AVI, respectively;
- $I_{Lph}, \cos \varphi_L$ – phase power at the output of the AVI and $\cos \varphi$ converter, measured by the “Power Meter” module, respectively.

f , Hz						Note
U_d , V						$R_L =$
I_d , A						
$U_{Lph(1)}$, V						
$I_{Lph(1)}$, A						
$P_{Lph(1)}$, Wt						
$\cos \varphi$						
P_d , Wt						
P_L , Wt						
P_L , Wt						
η_L						
μ						

Таблица 4

Output power

$$P_d = U_d \cdot I_d \quad (5)$$

Active and full power at load

$$P_L = 3 \cdot P_{Lph}, \quad S_L = 3 \cdot U_{Lph} \cdot I_{Lph} \quad (6)$$

Efficiency coefficient AVI

$$\eta_L = P_L / P_d \quad (7)$$

Modulation factor

$$\mu = \frac{\sqrt{3}\sqrt{2}U_{Lph(1)}}{U_d} \quad (8)$$

- (e) repeat experiment 2d with a different value of R_L specified by the teacher. Based on the data of experiments 2d, 2e construct the dependences $U_{Lph(1)} = F(f); \mu = F(f); P_d = F(f); P_L = F(f); S_L = F(f); \cos \varphi_L = F(f); \eta = F(f);$
- (f) take the external $U_{Lph(1)} = FI_{Lph}$ and the energy characteristics $P_d = F(I_{Lph}); P_L = F(I_{Lph}); S_L = F(I_{Lph}); \cos \varphi_L = F(I_{Lph}); \eta = F(I_{Lph})$ of an autonomous voltage inverter at a given frequency value f . To do this, use potentiometer $RP1$ in the “Frequency Converter” module to set the set frequency value f (frequency according to the device) and change the load current I_{Lph} with switch $SA1$ in the “Load” module. Record the same values as in experiment 2d, as well as the value of R_L . Enter the data into the table 5;
- (g) repeat experiment 2f with a different value of f specified by the teacher. Based on the data of experiments 2f, 2g construct the dependences $U_{Lph(1)} = FI_{Lph}, P_d = F(I_{Lph}); P_L = F(I_{Lph}); S_L = F(I_{Lph}); \cos \varphi_L = F(I_{Lph}); \eta = F(I_{Lph}).$

Turn off the $SA1$ toggle switch of the “Frequency Converter” module, the “Network” toggle switch of the “Power Meter” module, as well as the $QF2$ “Power Module” and $QF1$ “Bench Power Module” circuit breakers.

1.5 Contents of the report

The report should contain the following points:

1. name and purpose of the work;
2. electrical circuit diagrams for performing experiments;

R_L , Ohm						Note
U_d , V						$f =$
I_d , A						
$U_{Lph(1)}$, V						
$I_{Lph(1)}$, A						
$P_{Lph(1)}$, Wt						
$\cos \varphi$						
P_d , Wt						
P_L , Wt						
P_L , Wt						
η_L						
μ						

Таблица 5

3. the results of experimental studies and calculations based on them, placed in the appropriate tables;
4. experimentally measured and constructed characteristics;
5. processed oscillograms;
6. comparison of experimental results and preliminary calculations;
7. conclusions from the work:
 - Indicate which modulation method is used in the AVI;
 - explain the influence of load current on the regulating characteristics of the AVI;
 - explain the influence of control frequency and load current on energy AVI indicators.

1.6 Control questions

1. What is the difference between a slave and an autonomous inverter?

2. What is the difference between an autonomous voltage inverter and an autonomous current inverter?
3. Why are reverse diodes turned on in voltage inverters?
4. Why is there a capacitor at the input of the AVI?
5. How to change the output frequency of a stand-alone inverter?
6. What depends on the carrier frequency?
7. Show the contours of current flow in a three-phase AVI.
8. How is the shape and magnitude of the voltage in the AVI regulated?
9. Compare the methods of generating phase voltages in three-phase AIN according to maximum achievable voltages and switching losses.
10. Which autonomous inverters are most promising in electric drives in present time?
11. What is the type of external characteristic of AVI? What does the slope of the characteristic depend on?
12. How to remove an external characteristic?
13. What is the regulating (frequency) characteristic of an autonomous inverter?
14. What type and why does the regulating (frequency) characteristic of the AVI for an electric drive have?
15. How to remove the adjustment (frequency) characteristic?
16. What determines the non-sinusoidal coefficient of the load current curve?
17. How to determine the efficiency of an AVI?
18. The procedure for turning on and off the laboratory installation.